

UNIVERSITY OF CALCUTTA

FAKIR CHAND COLLEGE

B.SC. PART-I (HONS.) SUPPLEMENTARY EXAMINATION : 2020

CMSA-PAPER : II B

F.M. : 50

TIME : 2 Hrs

PRACTICAL

Answer the following questions:

5x10=50

1. Draw and give the truth table for FULL ADDER
2. Draw and give the truth table for FULL SUBTRACTOR
3. Draw and give the truth table for 4:1 MULTIPLEXER
4. Draw and give the truth table for 2 bit MULTIPLIER
5. Draw and give the truth table for 3:8 DECODER