

UNIVERSITY OF CALCUTTA

FAKIR CHAND COLLEGE

B.SC. PART-I (HONS.) SUPPLEMENTARY EXAMINATION : 2020

CMSA-PAPER : I

F.M. : 100

TIME : 4 Hrs

1. **Answer any four questions :** 4 X 5 = 20
 - a) What are input devices ? Give example.
 - b) Distinguish between Rom and Ram.
 - c) Convert the following Binary code to its equivalent Gray code: 1101
 - d) What is the function of PC?
 - e) What are the differences between edge triggered and level triggered flip-flop?
 - f) What are the differences between EPROM and EEPROM?
 - g) Explain the working of a full wave bridge rectifier with diagram?
 - h) Explain the working of zener diode as a voltage regulator with diagram?

2. **Answer any four questions :** 4 X 20 = 80
 - a) Explain all the generations of computer.
 - b) Explain the De Morgan's theorem .
 - c) What is CMRR of OPAMP? Draw and explain the working of OPAMP as a Schmitt trigger?
 - d) Draw and explain the working of zero crossing detector? State Thevenin's theorem?
 - e) Design full adder and full subtractor using Decoder.
 - f) Design Mod-4 synchronous counter.
 - g) Draw the flow chart of instruction cycle.
 - h) Explain about addressing mode.