

FAKIR CHAND COLLEGE
ELECTRONIC SCIENCE – GENERAL - 2020
Part-II

Full Marks-50

Time- 2 hours

Group-A

Answer question no.1 and any other two questions.

1. Answer any 5 questions: **1x5**
 - (a) What is the decimal equivalent of $(1010.011)_2$?
 - (b) What are the basic differences between a decoder and a demultiplexer?
 - (c) Verify the Boolean identity: $A(A+B)=A$.
 - (d) What is Parity bit and in what purpose it is used?
 - (e) Convert $(BC56)_{16}$ to octal number system?
 - (f) What are the basic components of unregulated power supply?
 - (g) What is meant deflection sensitivity?
 - (h) What is a multimeter?
2. (a) Design a full adder circuit using 4:1 MUX. **6**
(b) Subtract $(1000100)_2$ from $(1010100)_2$ using 2's complement method. **4**
3. (a) Simplify the Boolean expression $F(A,B,C,D)=\sum m(3,4,5,7,9,13,14,15)$ USING Karnaugh map. **4**
(b) Draw a circuit diagram of 4-bit ripple counter and give its timing diagram. **6**
4. (a) Draw a circuit of D flip-flop with NAND gates. Write its truth table. **2+1**
(b) Draw and explain the circuit of a 4 bit shift register with serial loading, parallel loading, serial reading and parallel reading. **7**
5. (a) Sketch the circuit diagram of L type, LC type and pi type filter. **2**
(b) What is meant by Load and Line regulation? **2**
(c) Draw the circuit diagram of regulated power supply using zener diode and explain its operation? **6**
6. Draw the block diagram of CRO. Explain with block diagram the principle of operation of sweep frequency generator. **5+5**
7. Draw the circuit diagram of triangular wave generator. Give the block diagram of a function generator. **5+5**

Group-B

Answer question no.8 and any two other questions.

8. Answer any 5 questions: **1x5**

- (a) What is dielectric polarization?
- (b) Define SNR.
- (c) What is meant by lossless transmission line?
- (d) What is demodulation?
- (e) What is PWM?
- (f) Write Poisson's equation.
- (g) State Coulomb's law.
- (h) What is self-inductance?

9. State Biot-Savart's law. Give integral and differential forms of Gauss's law in electrostatics.

Find an expression for the energy stored in a charged capacitor. **2+4+4**

10. (a) What are meant by electric displacement and electric polarization? Write the relation between them. **5**

(b) What is an electric dipole? Find the electric field of an electric dipole at a distance r from origin. **5**

11. What is transmission line? Derive transmission line equations in terms of voltage and current and its solutions. What is meant by characteristic impedance of a transmission line? **2+6+2**

12. (a) Define reflection co-efficient of a transmission line. What would its value be for a open circuited, short circuited and perfectly matched line? **2+3**

(b) What is a standing wave? Define VSWR for a lossless transmission line. How is it related to reflection co-efficient? **2+2+1**

13. What are the different ways in which a radio wave can travel from a transmitting antenna to receiving antenna? Why is sky wave reception better at night? What are cut-off wavelength and guide wavelength? **4+3+3**

14. Obtain the expression for AM wave. Sketch the waveform of message signal, carrier signal and AM wave. What are modulation envelope and over modulation? **5+1+4**

15. (a) the peak to peak value of an AM voltage has a maximum value of 8V and a minimum voltage of 2V. What are the percentage of modulation and the amplitude of the modulated carrier? **5**

(b) Describe the side bands present in an FM wave. Compare these side bands with those of AM wave. **2+3**